
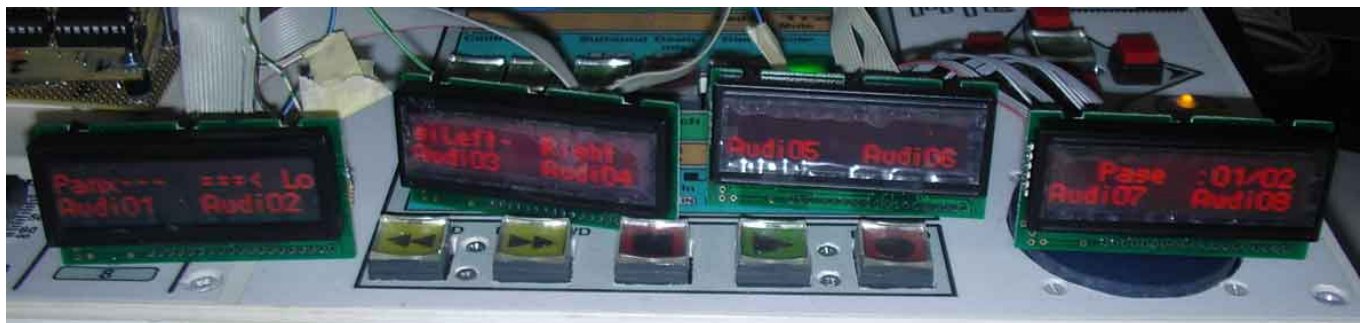


Driving a MIDIBox LC with 4 LCDs on 1 CORE

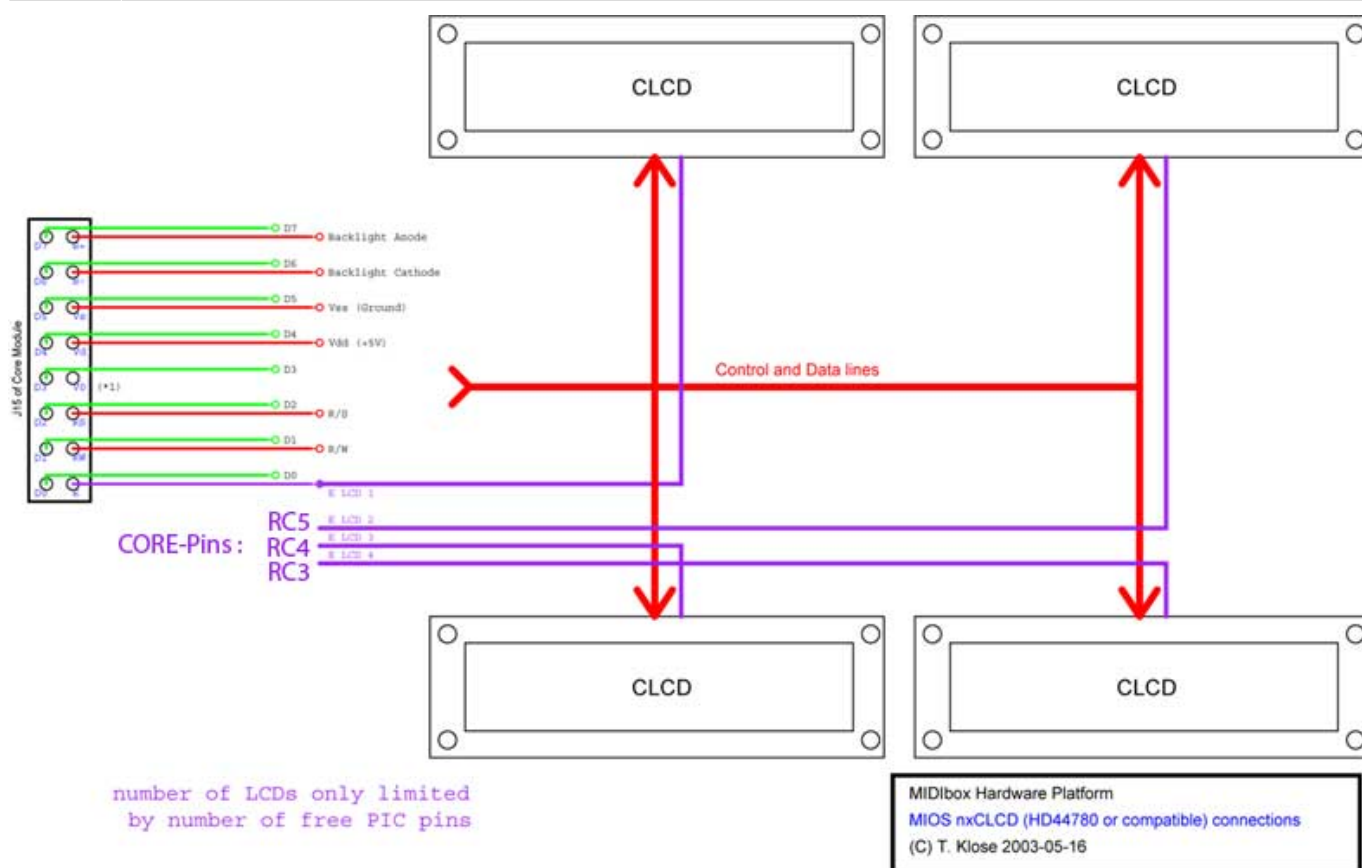The idea was to drive a LC with 4 (2×16 characters) LCDs to have the optimal spreading of the names & values on the 8 Channels, so use for a pair of 2 Channels 1 LCD ;)



How to connect



!! IMPORTANT NOTES !!

If you get strange reboots or the LCDs wont work correct, remove Resistor R10 !

Also if you have 4-bit LCDs, [dont connect D0 - D3](#)

Firmware

[Download](#)

From:
<http://www.midibox.org/dokuwiki/> - **MIDibox**

Permanent link:
http://www.midibox.org/dokuwiki/doku.php?id=drive_a_midibox-lc_with_4_lcds_on_1_core

Last update: **2011/09/17 01:00**