Written as I=V/R where I is the current flowing, V is the voltage and R is the resistance.

From:
https://www.midibox.org/dokuwiki/ - **MIDIbox**

Permanent link:
https://www.midibox.org/dokuwiki/doku.php?id=ohm_s_law&rev=1160904901

Last update: **2011/08/23 07:13**